

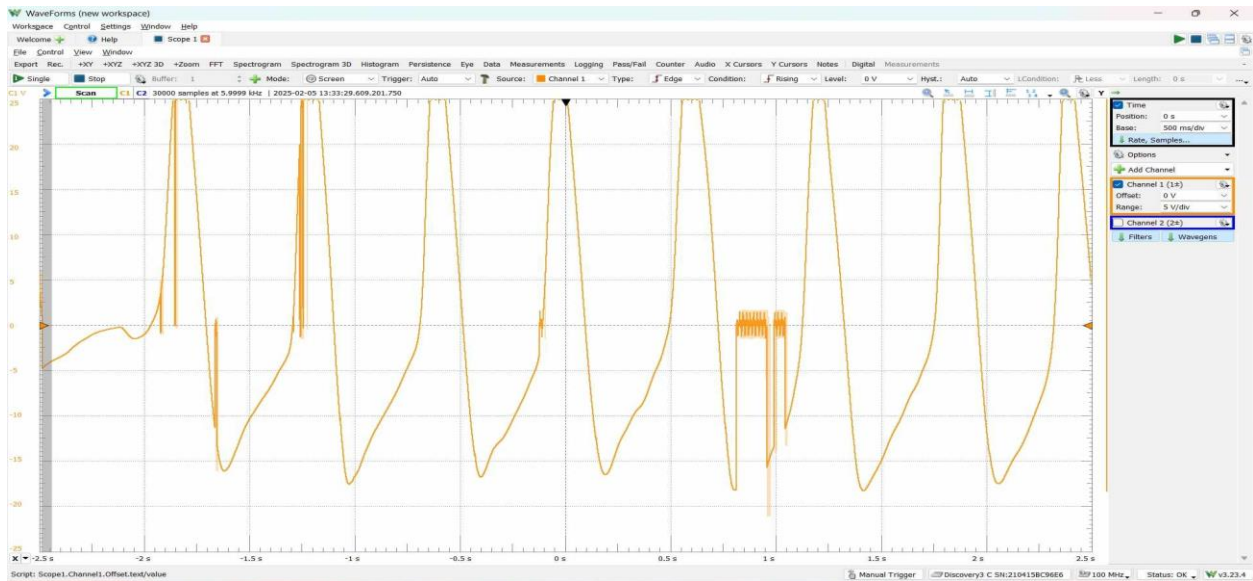


“AC”

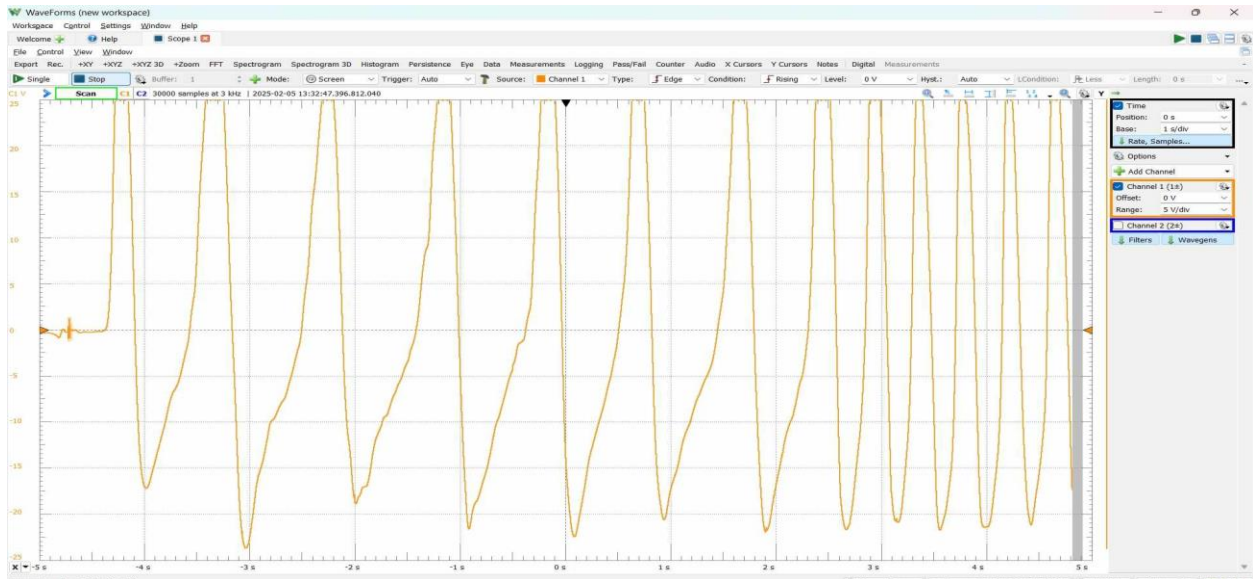

This result generates while testing the piezoelectric sensor alone in an AC circuit with a 5V signal and 500ms and 1s pulse while using the Analog Discovery 3. This test checks the sensor's responsiveness to the input signal.

“DC”

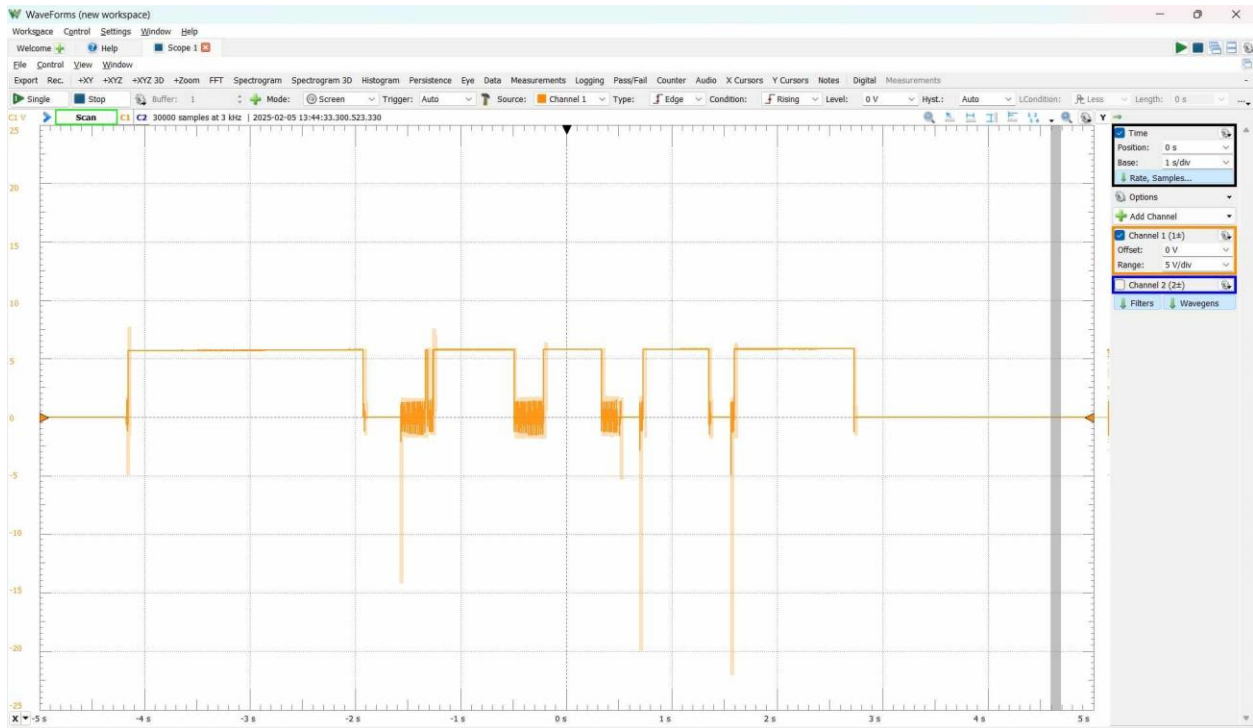

This waveform generates when the piezoelectric sensor received mechanical stress ranging with a 5V and 1 second pulse using the Analog Discovery 3. The sensor will generate an AC voltage, which is rectified by the diode to produce a DC signal. The waveform or voltage drop because it filtered by the diode bridge rectifier.